



INDIAN INSTITUTE OF INFORMATION TECHNOLOGY, NAGPUR

Department of Electronics and Communication Engineering

Academic Session: JULY to DECEMBER (Odd Semester)

CMOS LAB (ECL-312)

V Semester ECE-IoT

Date:30/07/2024

Experiment No.1.1

Aim: To perform analysis of Voltage Divider circuit.

Software Required: WinSpice.

Theory:

DC ANALYSIS: It is used for analysis of static characteristics like voltage drops , current flows etc. and is important for understanding the overall performance and functionality of a circuit.

AC ANALYSIS: It mainly addresses characteristics related to frequency , including impedance, reactance and resonance which is essential for designing and optimizing filters, amplifiers and communication systems.

TRANSIENT ANALYSIS: It is used to study the time-dependent behavior of circuits, including their response to sudden changes in inputs, switching events and disturbances ensuring stability, performance and reliability in real world conditions.

Codes:

I. DC ANALYSIS:

```
***DC Analysis***  
V1 2 0 5V  
R1 2 1 8K  
R2 1 0 2K  
.dc V1 0.0 5.0 0.1  
.control  
run  
plot V(1) V(2)  
.endc  
.end
```

II. AC ANALYSIS:


```
***AC Analysis***  
V1 2 0 dc 0 ac 5  
R1 2 1 8K  
R2 1 0 2K  
.ac dec 10 1 10K  
.control  
run  
plot V(1) V(2)  
.endc  
.end
```

III. TRANSIENT ANALYSIS:


```
***TRAN Analysis***  
V1 2 0 pulse( 0 5 0 0 0 1 100m 200m)  
R1 2 1 8K  
R2 1 0 2K  
.tran 0.1m 400m V1 0.0 5.0 0.1  
.control  
run  
plot V(1) V(2)  
.endc  
.end
```

Output:


I. DC ANALYSIS:

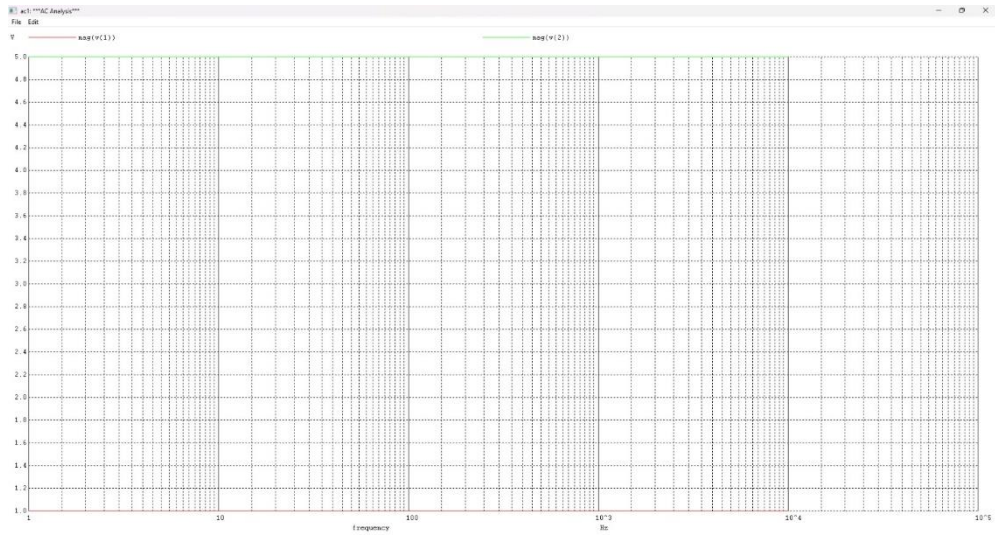

II. AC ANALYSIS:

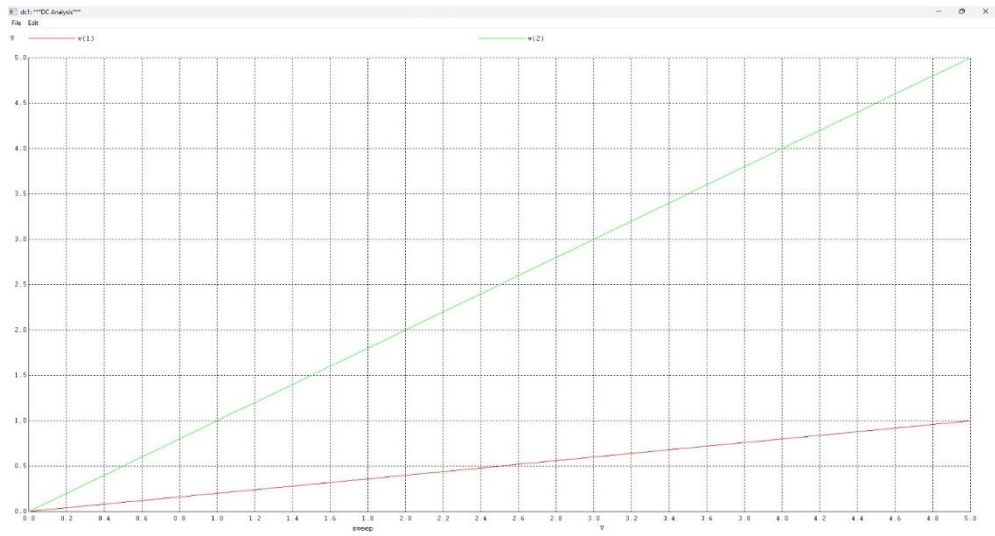

III. TRANSIENT ANALYSIS:

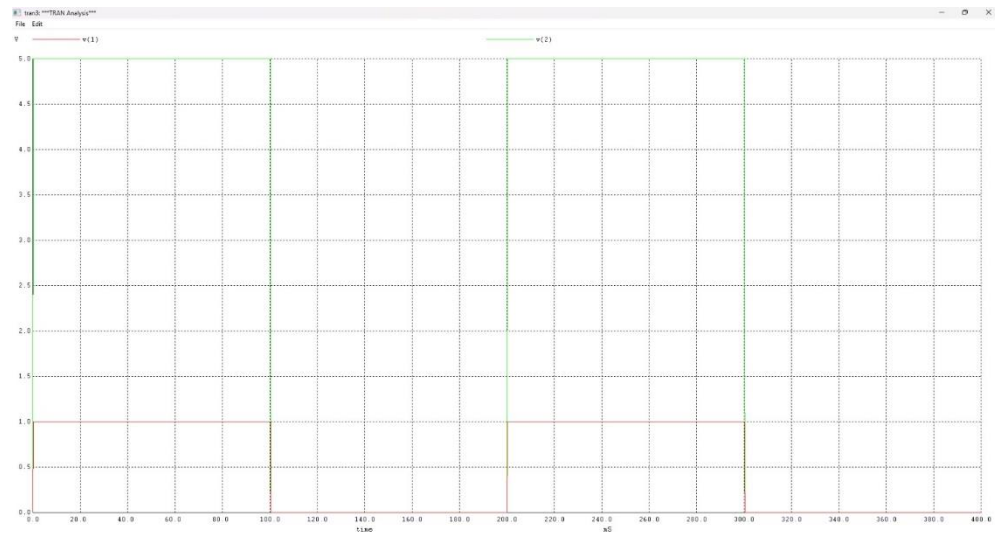

Result/ Conclusion:

We have successfully stimulated the Voltage Divider Circuit and performed all types of analysis.