



# INDIAN INSTITUTE OF INFORMATION TECHNOLOGY, NAGPUR

Department of Electronics and Communication Engineering

Academic Session: JULY to DECEMBER (Odd Semester)

**CMOS LAB (ECL-312)**

V Semester ECE-IoT

---

Date:19/08/2024

## Experiment No.4

**Aim:** To design CMOS circuit for the given equations using sub-circuit approach.

**Software Required:** WinSpice.

### **Theory:**

#### **CMOS Logic Gates**

- **CMOS Inverter:** The basic building block of CMOS technology is the inverter, which consists of one PMOS and one NMOS transistor.
- **CMOS NAND and NOR Gates:** More complex logic gates like NAND and NOR can be built by combining multiple PMOS and NMOS transistors.

**Sub-Circuit Approach** The sub-circuit approach involves breaking down a complex Boolean expression into simpler sub-expressions that can be realized using basic CMOS logic gates. Each sub-expression is designed separately as a sub-circuit, which is then combined to form the overall circuit.

## Codes:

### I. $Y=ABC+D$ :

```
**abc+d**  
.subckt pass_and 1 2 3 4  
M1 1 2 4 4 nmod w=100u l=10u  
M2 2 3 4 4 nmod w=100u l=10u  
.model nmod nmos level=54 version=4.7  
.ends  
.subckt pass_or 1 2 3 4  
M1 2 2 4 4 nmod w=100u l=10u  
M2 1 3 4 4 nmod w=100u l=10u  
.model nmod nmos level=54 version=4.7  
.ends  
.subckt pass_inv 1 2 3  
M1 3 1 0 0 pmod w=100u l=10u  
M2 3 1 2 2 nmod w=100u l=10u  
.model nmod nmos level=54 version=4.7  
.model pmod pmos level=54 version=4.7  
.ends  
Va 10 0 pulse(0 5 0 0 0 100m 200m)  
Vb 11 0 dc 5  
Vc 14 0 dc 5  
Vd 17 0 dc 0  
Vdd 2 0 dc 5  
Xb 11 2 12 pass_inv  
Xc 14 2 15 pass_inv  
Xd 17 2 18 pass_inv  
Xa_and_b 10 11 12 13 pass_and  
Xab_and_c 13 14 15 16 pass_and  
Xabc_or_d 16 17 18 19 pass_or  
.tran 0.1m 400m  
.control  
run  
plot v(10) v(19)  
.endc  
.end
```

## II. $Y=(AB+C)D$ :

**\*\* $(AB+C)D$ \*\***

.subckt pass\_and 1 2 3 4

M1 1 2 4 4 nmod w=100u l=10u

M2 2 3 4 4 nmod w=100u l=10u

.model nmod nmos level=54 version=4.7

.ends

.subckt pass\_or 1 2 3 4

M1 2 2 4 4 nmod w=100u l=10u

M2 1 3 4 4 nmod w=100u l=10u

.model nmod nmos level=54 version=4.7

.ends

.subckt pass\_inv 1 2 3

M1 3 1 0 0 pmod w=100u l=10u

M2 3 1 2 2 nmod w=100u l=10u

.model nmod nmos level=54 version=4.7

.model pmod pmos level=54 version=4.7

.ends

Vdd 2 0 dc 5

Va 10 0 pulse(0 5 0 0 0 100m 200m)

Vb 11 0 dc 5

Vc 14 0 dc 5

Vd 17 0 dc 5

Xb 11 2 12 pass\_inv

Xc 14 2 15 pass\_inv

Xd 17 2 18 pass\_inv

Xa\_and\_b 10 11 12 13 pass\_and

Xab\_or\_c 13 14 15 16 pass\_or

Xab\_c\_and\_d 16 17 18 19 pass\_and

.tran 0.1m 400m

.control

run

plot v(10) v(19)

.endc


.end

### III. $Y=AB+C(D+E)$ :


```
.subckt pass_and 1 2 3 4
M1 1 2 4 4 nmod w=100u l=10u
M2 2 3 4 4 nmod w=100u l=10u
.model nmod nmos level=54 version=4.7
.ends
.subckt pass_or 1 2 3 4
M1 2 2 4 4 nmod w=100u l=10u
M2 1 3 4 4 nmod w=100u l=10u
.model nmod nmos level=54 version=4.7
.ends
.subckt pass_inv 1 2 3
M1 3 1 0 0 pmod w=100u l=10u
M2 3 1 2 2 nmod w=100u l=10u
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.ends
Vdd 2 0 dc 5
Va 10 0 pulse(0 5 0 0 0 100m 200m)
Vb 11 0 dc 5
Vc 14 0 dc 5
Vd 17 0 dc 5
Ve 20 0 dc 5
Xb 11 2 12 pass_inv
Xc 14 2 15 pass_inv
Xd 17 2 18 pass_inv
Xe 20 2 21 pass_inv
Xa_and_b 10 11 12 13 pass_and
Xd_and_e 17 20 21 22 pass_or
Xc_and_de 14 22 23 24 pass_and
Xab_or_cde 13 24 25 26 pass_or
.tran 0.1m 400m
.control
run
plot v(10) v(26)
.endc
.end
```

## Output:


### I. $Y=ABC+D$ :

 

### II. $Y=(AB+C)D$ :

 

### III. $Y=AB+C(D+E)$ :

 

#### Result/ Conclusion:

By following the sub-circuit approach, complex CMOS circuits can be designed in a modular manner, which simplifies the design process and improves the accuracy of the final circuit. This lab exercise provides practical experience in CMOS circuit design and verification.